
PHYS 1120 Discussion 8.

Phasors

In an alternating current (ac) circuit, the volage from the power supply is $V = V_S \sin(\omega t)$. This can be visualized as the y -component of a vector of constant magnitude V_S rotating at constant angular speed ω , so that its angular position at time t is ωt . Such a vector is known for short as a **phasor**.


Resistors

In a resistor, Ohm's law tells us that the current is directly proportional to the voltage: $I = V/R$. This, for a resistor, the current phasor I always points in the same direction as the voltage phasor V_R : the current and voltage are *in phase*.

Capacitors

In a capacitor, charge, not current, is proportional to voltage: $Q = CV$. This means that the charge phasor Q is in phase with the voltage phasor V . The current, on the other hand, is the rate of change of the charge: $I = \Delta Q/\Delta t$. We can think of $\Delta Q/\Delta t$ as the velocity of the phase vector Q . What we know of uniform circular motion tells us that the speed of something rotating at angular speed ω in a circular path of radius r is ωr . Here, the current I is rotating at angular speed ω with radius $Q_0 = CV_S$. Its speed must be $\omega Q_0 = \omega CV_S$.

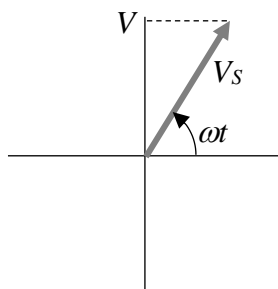Below is a representation of the voltage phasor V at some particular time.



1. Draw a representation of the charge phasor Q at that same time.
2. What is the magnitude Q_0 of the charge phasor Q ?
3. Draw a representation of the current phasor I at that time. Remember that the current phasor is the velocity of the charge phasor.

Notice that the current phasor *leads* the voltage phasor by $\frac{1}{4}$ cycle.

4. What is the magnitude I_0 of the current phasor?
5. What is the formula for the y -component of the current phasor at time t ? (The current is just the y -component of the current phasor.)

We'd like to extend Ohm's law to apply to the voltage and current in a capacitor. As Ohm's law tells us $V = IR$, we'd like to define a quantity of the capacitor, its reactance X_C , that relates its current and voltage as $V = IX_C$.


6. What is the reactance of a capacitor with capacitance C in a circuit whose voltage varies at angular frequency ω ?

Inductors

How about an inductor? In an inductor, the voltage $V_L = L \Delta I / \Delta t$, so V_L / L is the velocity of the current phasor I . We want to find the magnitude of I . This will require some backward analysis.

In uniform circular motion, speed v is related to radius R and angular speed ω as $v = \omega R$. If we know v and ω , we can find $R = v / \omega$. Here, we have a speed of V_L / L and an angular speed of ω .

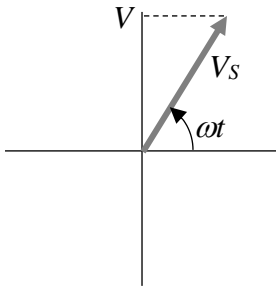7. What is the "radius" I_0 ? This value is the maximum current through the inductor, or the magnitude of the current phasor. Simplify the expression.
8. What is the direction of phasor I ? Below is a representation of the voltage phasor V at some time; Draw a representation of the phasor I at that time.



9. What is the formula for the y-component of the current phasor at time t ? (The current is just the y-component of the current phasor.)

We'd like to extend Ohm's law to apply to inductors, defining inductive reactance X_L much as capacitive reactance above: $V = IX_L$.

10. What is the reactance of an inductor with inductance L in a circuit whose voltage varies at angular frequency ω ?

Notice that the current phasor in an inductor *lags* the voltage phasor by $1/4$ cycle.

Reactance and Resistance

When a resistor is in series with a capacitor or inductor in an ac circuit, the current is always the same through all components, though their voltages are in different phases. I don't want to slog through that trigonometry now, but what we know gives us a way to find the reactance of a capacitor or inductor if we can measure the rms voltages of both it and the resistor in series. Because the current is the same, $I = V_R / R = V_X / X$, so $X = R V_X / V_R$.

Reactance and Resonance

An ac circuit will **resonate** when the capacitive reactance equals the inductive reactance.

11. At what angular frequency ω is the inductive reactance X_L of an inductor with inductance L equal to the capacitive reactance X_C of a capacitor with capacitance C ?