

## PHYS 1120 Discussion 8.

### Phasors

In an alternating current (ac) circuit, the volage from the power supply is  $V = V_S \sin(\omega t)$ . This can be visualized as the  $y$ -component of a vector of constant magnitude  $V_S$  rotating at constant angular speed  $\omega$ , so that its angular position at time  $t$  is  $\omega t$ . Such a vector is known for short as a **phasor**.


### Resistors

In a resistor, Ohm's law tells us that the current is directly proportional to the voltage:  $I = V/R$ . This, for a resistor, the current phasor  $I$  always points in the same direction as the voltage phasor  $V_R$ : the current and voltage are *in phase*.
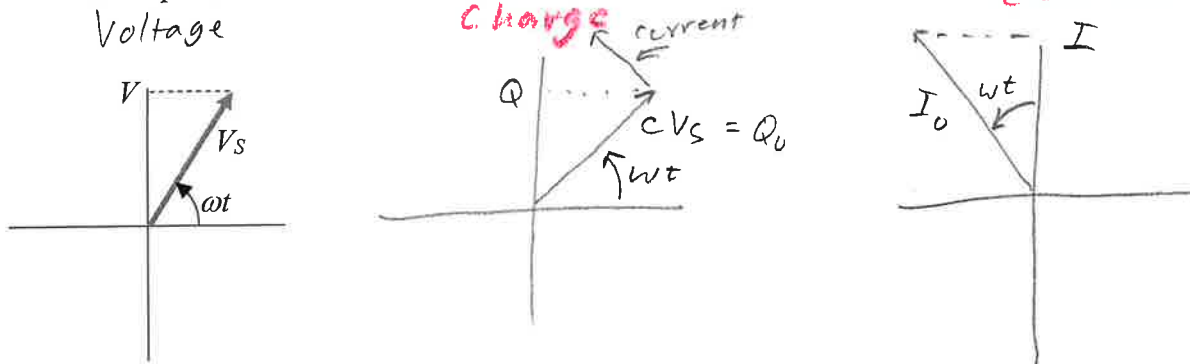
### Capacitors

In a capacitor, charge, not current, is proportional to voltage:  $Q = CV$ . This means that the charge phasor  $Q$  is in phase with the voltage phasor  $V$ . The current, on the other hand, is the rate of change of the charge:  $I = \Delta Q/\Delta t$ . We can think of  $\Delta Q/\Delta t$  as the velocity of the phase vector  $Q$ . What we know of uniform circular motion tells us that the speed of something rotating at angular speed  $\omega$  in a circular path of radius  $r$  is  $\omega r$ . Here, the current  $I$  is rotating at angular speed  $\omega$  with radius  $Q_0 = CV_S$ . Its speed must be  $\omega Q_0 = \omega CV_S$ .

Below is a representation of the voltage phasor  $V$  at some particular time.



1. Draw a representation of the charge phasor  $Q$  at that same time.
2. What is the magnitude  $Q_0$  of the charge phasor  $Q$ ?  $Q_0 = CV_S$
3. Draw a representation of the current phasor  $I$  at that time. Remember that the current phasor is the velocity of the charge phasor.

Notice that the current phasor *leads* the voltage phasor by  $\frac{1}{4}$  cycle.

4. What is the magnitude  $I_0$  of the current phasor?  $I_0 = \omega CV_S$
5. What is the formula for the  $y$ -component of the current phasor at time  $t$ ? (The current is just the  $y$ -component of the current phasor.)

$$I = \omega CV_S \cos(\omega t)$$

We'd like to extend Ohm's law to apply to the voltage and current in a capacitor. As Ohm's law tells us  $V = IR$ , we'd like to define a quantity of the capacitor, its reactance  $X_C$ , that relates its current and voltage as  $V = IX_C$ .

6. What is the reactance of a capacitor with capacitance  $C$  in a circuit whose voltage varies at angular frequency  $\omega$ ?

$$V_s = X_C I_0 = X_C \omega C V_s, \text{ so } \boxed{X_C = \frac{1}{\omega C}}$$


## Inductors

How about an inductor? In an inductor, the voltage  $V_L = L \Delta I / \Delta t$ , so  $V_L / L$  is the velocity of the current phasor  $I$ . We want to find the magnitude of  $I$ . This will require some backward analysis.

In uniform circular motion, speed  $v$  is related to radius  $R$  and angular speed  $\omega$  as  $v = \omega R$ . If we know  $v$  and  $\omega$ , we can find  $R = v / \omega$ . Here, we have a speed of  $V_L / L$  and an angular speed of  $\omega$ .

$$I = (V_L / L) / \omega = V_L / (\omega L)$$

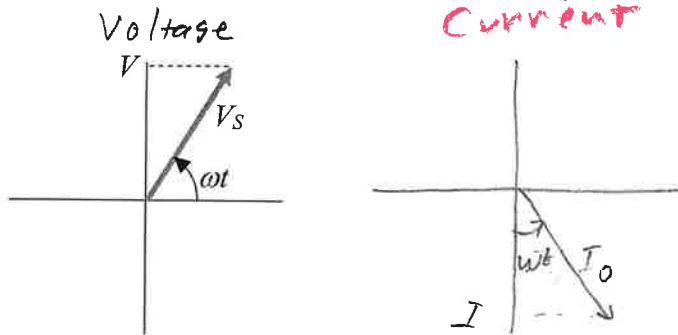7. What is the "radius"  $I_0$ ? This value is the maximum current through the inductor, or the magnitude of the current phasor. Simplify the expression.  $I_0 = V / (\omega L)$
8. What is the direction of phasor  $I$ ? Below is a representation of the voltage phasor  $V$  at some time; Draw a representation of the phasor  $I$  at that time.



9. What is the formula for the y-component of the current phasor at time  $t$ ? (The current is just the y-component of the current phasor.)  $I = -I_0 \cos(\omega t) = \frac{-V}{\omega L} \cos(\omega t)$

We'd like to extend Ohm's law to apply to inductors, defining inductive reactance  $X_L$  much as capacitive reactance above:  $V = IX_L$ .

10. What is the reactance of an inductor with inductance  $L$  in a circuit whose voltage varies at angular frequency  $\omega$ ?  $X_L = V / I = \boxed{\omega L}$

Notice that the current phasor in an inductor *lags* the voltage phasor by  $\frac{1}{4}$  cycle.

## Reactance and Resistance

When a resistor is in series with a capacitor or inductor in an ac circuit, the current is always the same through all components, though their voltages are in different phases. I don't want to slog through that trigonometry now, but what we know gives us a way to find the reactance of a capacitor or inductor if we can measure the rms voltages of both it and the resistor in series. Because the current is the same,  $I = V_R / R = V_X / X$ , so  $X = R V_X / V_R$ .

## Reactance and Resonance

An ac circuit will **resonate** when the capacitive reactance equals the inductive reactance.

11. At what angular frequency  $\omega$  is the inductive reactance  $X_L$  of an inductor with inductance  $L$  equal to the capacitive reactance  $X_C$  of a capacitor with capacitance  $C$ ?

$$\omega L = \frac{1}{\omega C}$$

$$\omega^2 = \frac{1}{LC}$$

$$\omega = \frac{1}{\sqrt{LC}}$$

